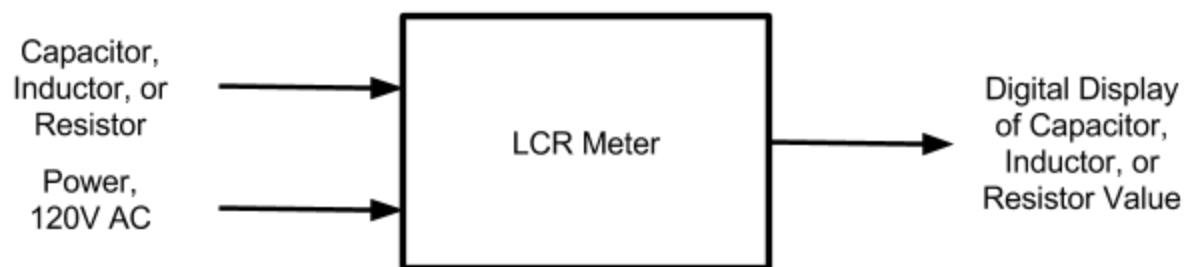


Kimi Owens  
Dario Lopez  
Celena Ponce  
Steven Bagdasarians  
ECE 411  
November 9, 2017


## Homework 5: Detailed Design

### Level 0 Block Diagram




<i>Module</i>	LCR Meter
<i>Inputs</i>	<ul style="list-style-type: none"><li>• Capacitor, resistor, or inductor to measure</li><li>• Power: 4.5 to 5.5V</li></ul>
<i>Outputs</i>	<ul style="list-style-type: none"><li>• Value of capacitor, resistor, or inductor</li></ul>
<i>Functionality</i>	Displays the value of a capacitor in Farads, a resistor in Ohms, or an inductor in Henrys on an LCD display screen

## Level 1 Block Diagram

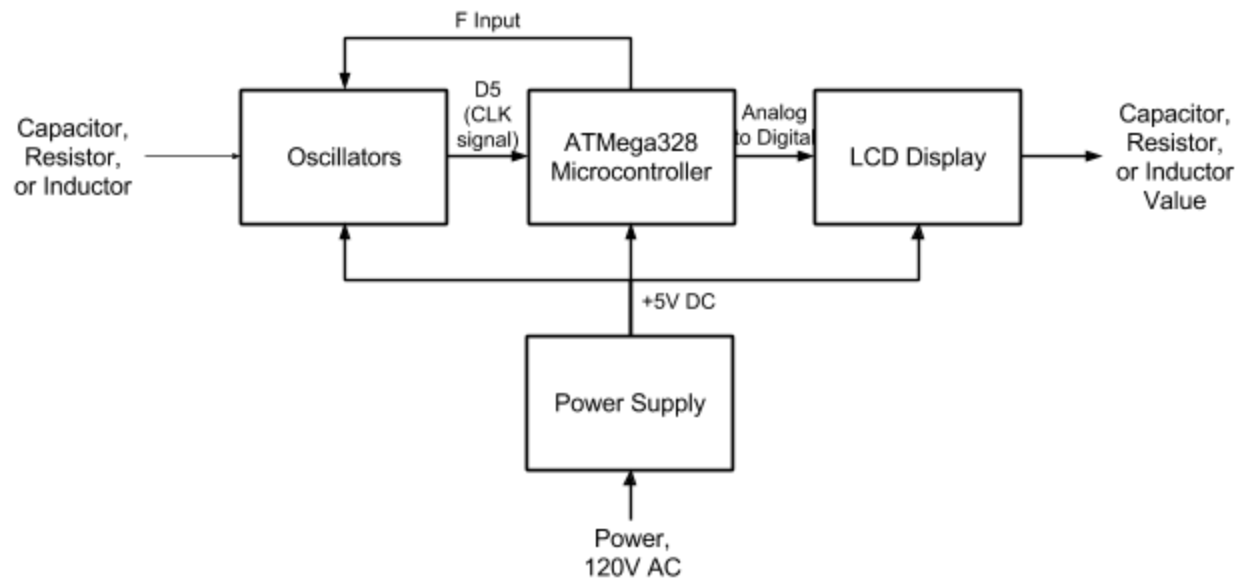

## Level 2 Block Diagram: Oscillators

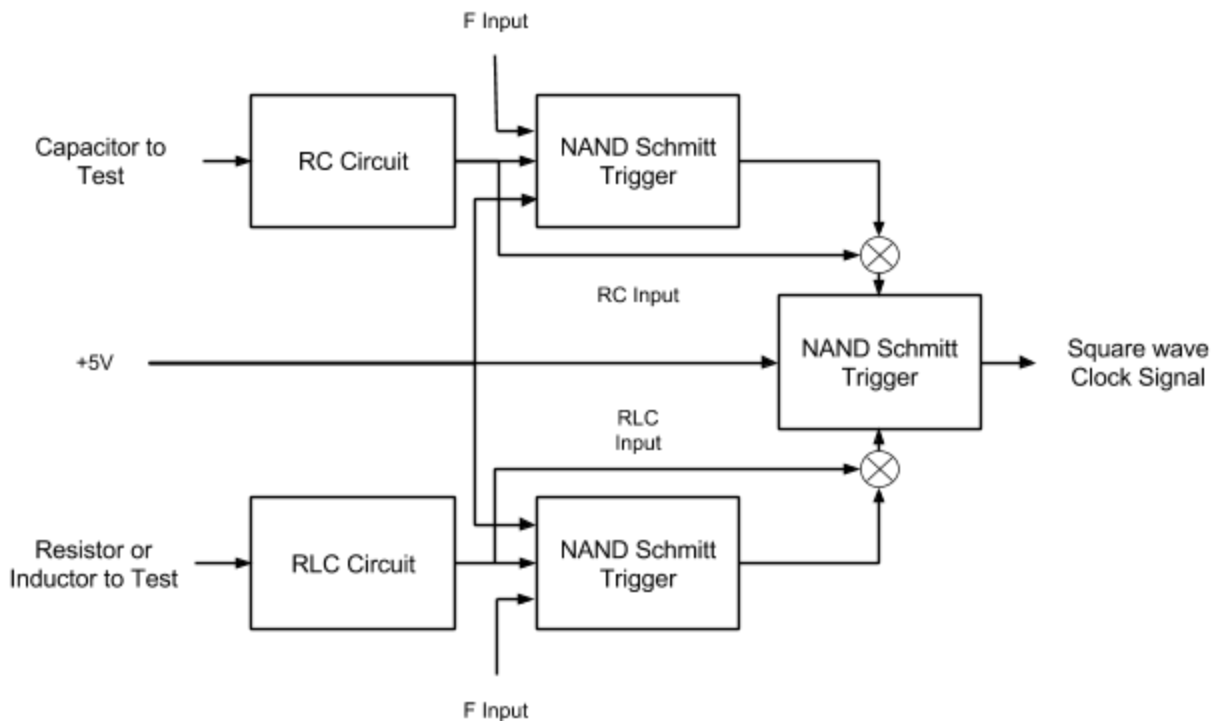


<i>Module</i>	RC Circuit
<i>Inputs</i>	<ul style="list-style-type: none"> <li>• Capacitor to measure</li> </ul>
<i>Outputs</i>	<ul style="list-style-type: none"> <li>• Change in impedance from RC circuit</li> </ul>
<i>Functionality</i>	Changes the input to the NAND Schmitt Trigger

<i>Module</i>	RLC Circuit
<i>Inputs</i>	<ul style="list-style-type: none"> <li>• Resistor or inductor to measure</li> </ul>
<i>Outputs</i>	<ul style="list-style-type: none"> <li>• Change in impedance from RLC circuit</li> </ul>
<i>Functionality</i>	Changes the input to the NAND Schmitt Trigger, which changes the output frequency of the NAND Schmitt Trigger

<i>Module</i>	Inductor Circuitry
<i>Inputs</i>	<ul style="list-style-type: none"> <li>• Inductor to measure</li> <li>• Power: 4.5 to 5.5V</li> </ul>
<i>Outputs</i>	<ul style="list-style-type: none"> <li>• Value of capacitor, resistor, or inductor</li> </ul>
<i>Functionality</i>	Changes the input to the NAND Schmitt Trigger, which changes the output frequency of the NAND Schmitt Trigger


<i>Module</i>	NAND Schmitt Trigger (74HC132)
<i>Inputs</i>	<ul style="list-style-type: none"> <li>• 5V power</li> <li>• F input from ATmega328</li> <li>• RLC input</li> </ul>
<i>Outputs</i>	<ul style="list-style-type: none"> <li>• D5(Arduino)</li> </ul>
<i>Functionality</i>	Changes the output frequency to a square wave clock signal
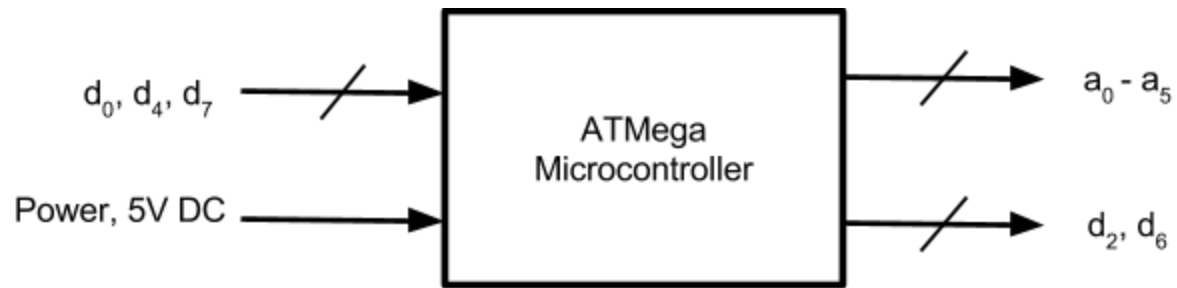
## Level 2 Block Diagram: ATmega Microcontroller




<i>Module</i>	ATmega Microcontroller
<i>Inputs</i>	<ul style="list-style-type: none"> <li>• <math>d_0</math>: Digital pin to select mode and positive calibration</li> <li>• <math>d_4</math>: Digital pin for negative calibration</li> <li>• <math>d_7</math>: Digital pin to set 0</li> <li>• 5V power supply</li> </ul>
<i>Outputs</i>	<ul style="list-style-type: none"> <li>• <math>a_0 - a_5</math>: Analog pins to LCD Display Screen</li> <li>• <math>d_2, d_6</math>: clock signals</li> </ul>
<i>Functionality</i>	Based on change of frequency from digital pins, the Arduino code calculates the resistor, inductor, or capacitor value
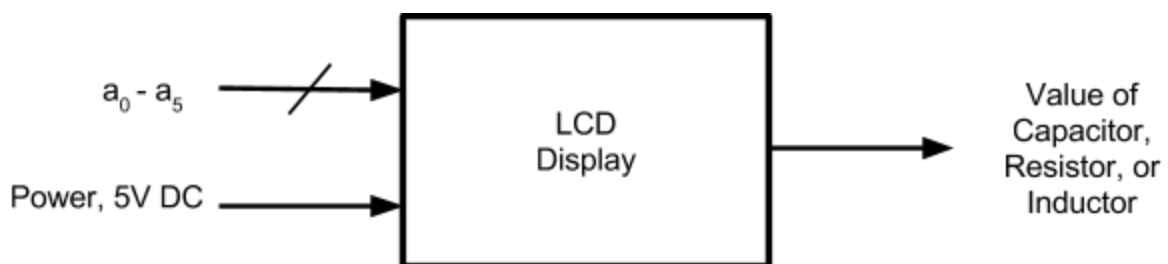
## Level 2 Block Diagram: LCD Display Screen



<i>Module</i>	LCD Display
<i>Inputs</i>	<ul style="list-style-type: none"> <li>• Power: 4.5 to 5.5V</li> <li>• <math>a_0 - a_5</math>: Analog pins to LCD Display Screen</li> </ul>
<i>Outputs</i>	<ul style="list-style-type: none"> <li>• Value of capacitor, resistor, or inductor</li> </ul>
<i>Functionality</i>	Displays the value of a capacitor in Farads, a resistor in Ohms, or an inductor in Henrys on an LCD display screen

## Level 2 Block Diagram: Power Supply

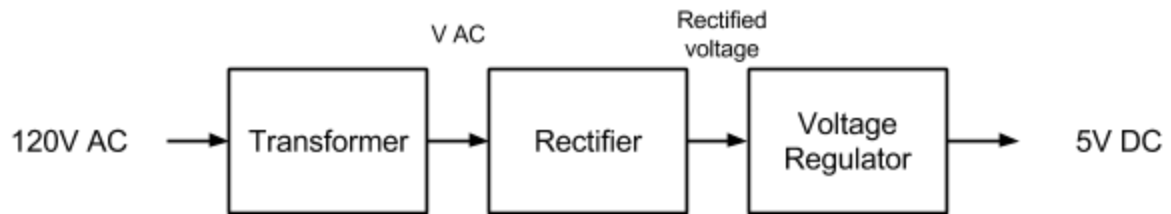

<i>Module</i>	Power Supply
<i>Inputs</i>	<ul style="list-style-type: none"><li>• 120V AC</li></ul>
<i>Outputs</i>	<ul style="list-style-type: none"><li>• 5V DC</li></ul>
<i>Functionality</i>	Converts the 120V AC from the wall input to 5V DC to power the circuit